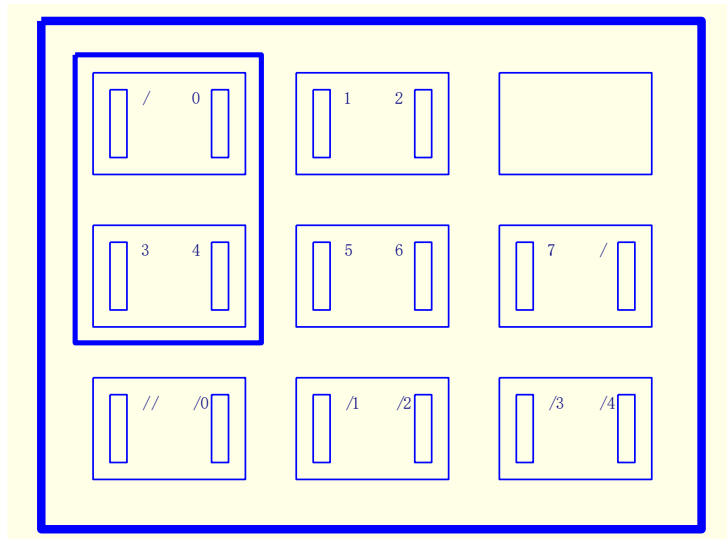


之



A/D D/A

U/F

F/U

JP11 JP12 JP13 JP14 JP15

220V

220V

±5V ±12V ±15V 0 30V

ON

OFF

220V

1

2

3

4

5

6

7

什 什
什

1 A_{ud} $CMRR$ U_{os} U_{oppm} I_{os} GW

2

3

4

1

2

3

4

1 U_{os} mV U_{os}

8-DIP


TO-99

2 3 6 7 4

8 1 5 1 5 5

1 5

1-1

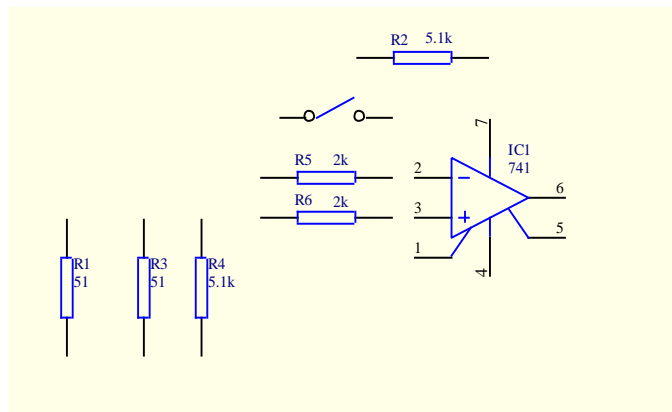

1-1

S1 S2

U_{O1}

$$A_{uf} = \frac{U_{O1}}{U_{OS}} = \frac{R_1 + R_2}{R_1}$$

$$U_{OS} = \frac{R_1}{R_1 + R_2} \cdot U_{O1} = \frac{1}{101} \cdot U_{O1} \quad 1-1$$

$$U_{OS} \quad \pm 1 \quad 20 \quad \text{mV} \quad U_{OS} \quad 1\text{mV}$$

2 I_{OS}

之

$$I_{OS} = |I_{B+} - I_{B-}|$$

I_{OS}

之

1-1

I_{OS}

S1 S2

U_{O1}'

$$I_{OS} = \frac{U_{O1}' - U_{O1}}{A_{uf} \cdot R_5} = \frac{R_1}{R_1 + R_2} \cdot \frac{U_{O1}' - U_{O1}}{R_5} \quad 1-2$$

I_{OS}

1nA

3

A_{ud}

ΔU_o

ΔU_{id}


$$A_{ud} = \frac{\Delta U_o}{\Delta U_{id}}$$

dB

$$A_{ud}(\text{dB}) = 20 \lg \left(\frac{\Delta U_o}{\Delta U_{id}} \right) \quad (\text{dB})$$

Hz

1-2

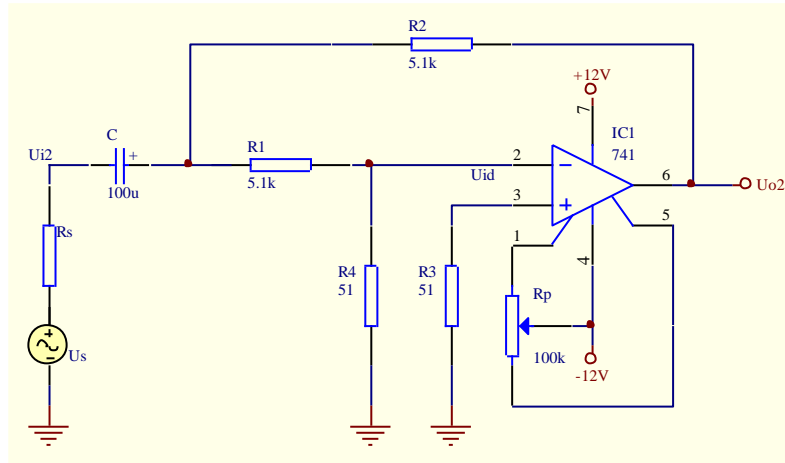

$$A_{ud} = \frac{R_2}{R_1} \cdot \frac{R_1 + R_4}{R_4} \cdot \frac{U_{o2}}{U_{id}} \quad (1-2)$$

$$A_{ud}(\text{dB}) = 20 \lg \left(\frac{\Delta U_{o2}}{\Delta U_{id}} \right) = 20 \lg \left[\left(1 + \frac{R_1}{R_4} \right) \cdot \frac{U_{O2}}{U_{i2}} \right] \cdot (\text{dB}) \quad (1-3)$$

100dB

4

CMRR

A_{ud}

A_{uc}

$$CMRR = \frac{A_{ud}}{A_{uc}}$$

dB

CMRR


$$CMRR = 20 \lg \left(\frac{A_{ud}}{A_{uc}} \right) (\text{dB})$$

CMRR 之

CMRR

1-3

CMRR

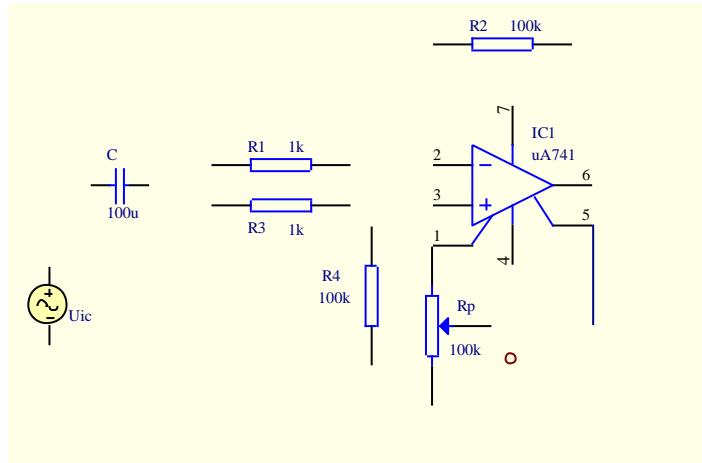

1-3 *CMRR*

$$|A_{ud}| = \frac{R_2}{R_1}$$

$$|A_{uc}| = \frac{U_{oc}}{U_{ic}}$$

CMRR

$$CMRR = 20 \lg \left(\frac{R_2 U_{ic}}{R_1 U_{oc}} \right) \text{ (dB)}$$


1-4

5

U_{oc} U_{ic} *CMRR* *CMRR* 80dB
 U_{oppm}
 U_{oppm}

10V

1-4

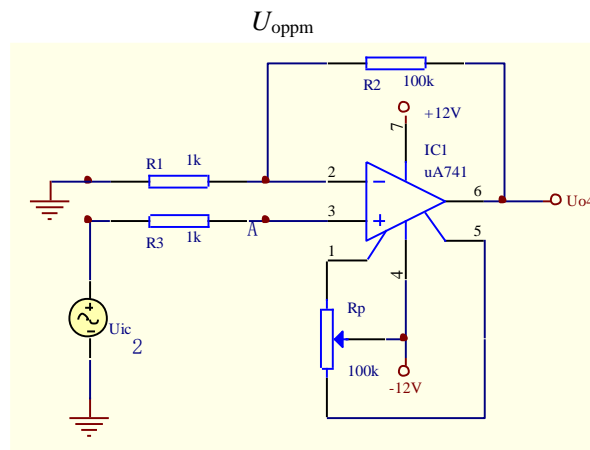

1-4

U_{oppm}

6

GW

GW
0.707

1

$$GW = A_{ud} f$$


1-5

GW

100~200mV

1-5

GW

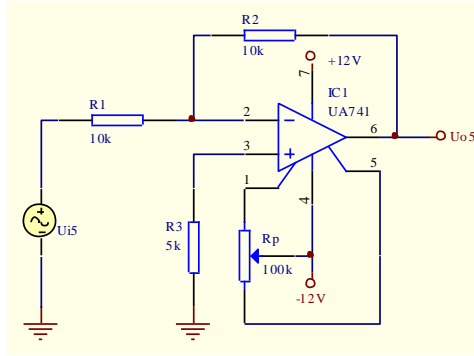

1-5

GW

1		U_{os}		I_{os}		
1	Sa	ON				
2	S1 S2					
U_{O1}	U_{O1}					
3	S1 S2					U_{O1}'
	U_{O1}'					
4		1-1	1-2	U_{Os}	I_{Os}	
		Sa	OFF			
2		A_{ud}				
1	Sb	ON				
2		U_{i2}		100Hz		50mV
		U_{O2}		U_{i2}	U_{O2}	
3		1-3	A_{ud}			
		Sb	OFF			
3		CMRR				
1	Sc	ON	S3 S5 S7			
2		U_{i3}		100Hz		1V
		U_{O3}		U_{i3}	U_{O3}	之
U_{O3}	U_{O3}	A1				
3		1-4	CMRR			
		Sc	OFF			
4		U_{oppm}				
1	Sc	ON	S4 S6 S8			
2		U_{i4}		100Hz		

U_{O4}
 U_{oppm}
5 Sc OFF
GW
 1 Sd ON
 2 U_{i5} 100mV
 SR2

$$A_u = \frac{U_{o5}}{U_{i5}} = 0.707$$

Sd OFF

1 U_{OS} I_{OS} A_{ud} $CMRR$ U_{oppm} GW
 2
 3

1 U_{OS} I_{OS}

2 U_{OS} I_{OS}

3

4


5

1
2

1
2
3
4

1 30

8-DIP TO-99

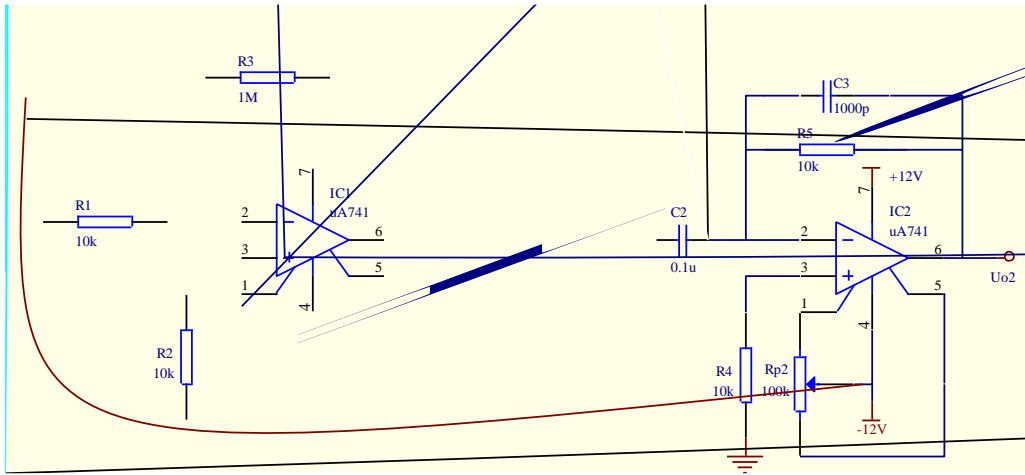

2-1

2-1 S1 IC1

$$u_{o1}(t) = -\frac{1}{R_1 C_1} \int u_{i1}(t) dt \quad 2-1$$

3


2-1 S1 S2 IC2

$$u_{o2}(t) = -R_5 C_2 \frac{du_{i2}(t)}{dt} \quad 2-2$$


4

2-1 S2 S1 IC1 IC2


1

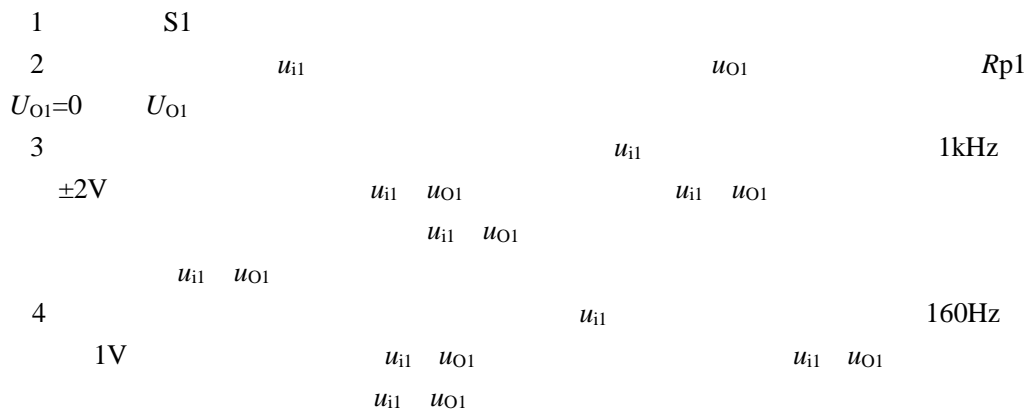

2

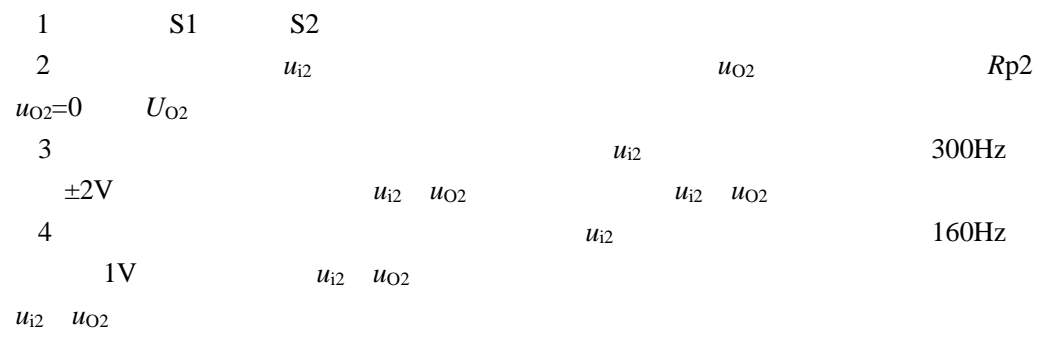

3

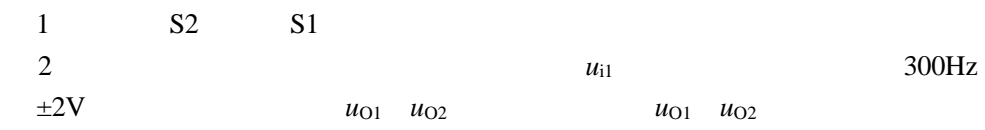

1

2

3

LM311

1
2 LM311
3

1
2
3
4
5

之

3

5ns

TTL ECL HTL NMOS PMOS

LM311

1 LM311

LM311

6.0nA

±30V

±5V ±15V

100nA

TTL DTL MOS

之

LM311

8-DIP

TO-99

3-1


LM311

3-1 LM311


1	GND	3	IN	5	BALANCE	7	OUT
2	IN+	4	V	6	BALANCE/STROBE	8	V+

2


3-1

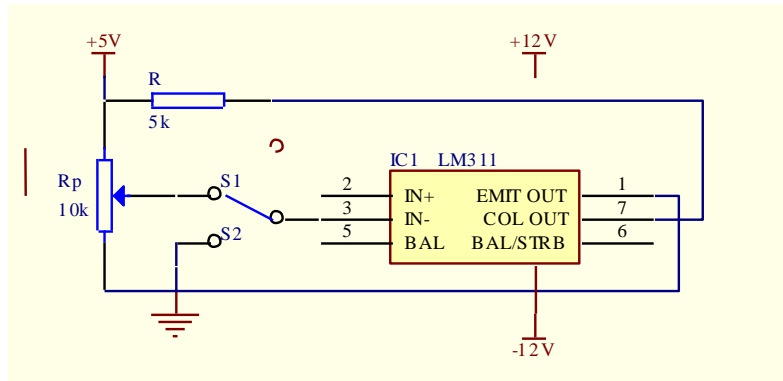


3-1

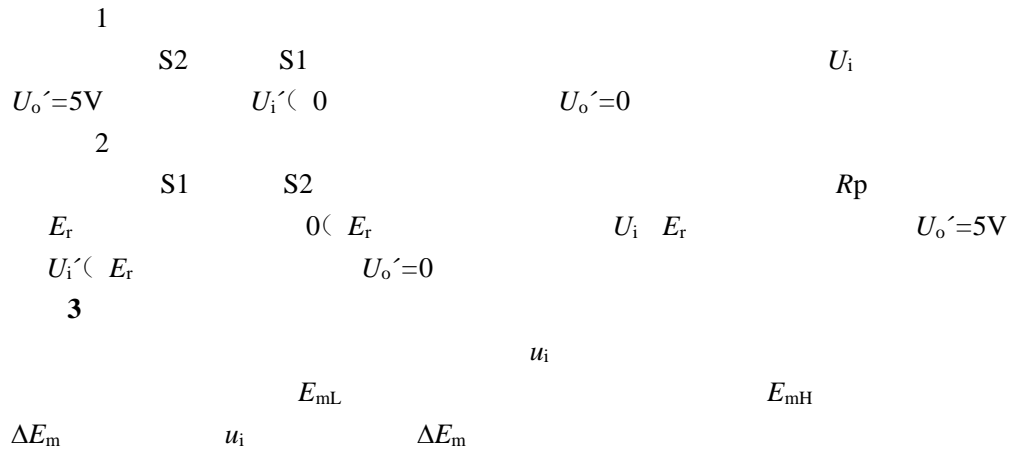

3-2

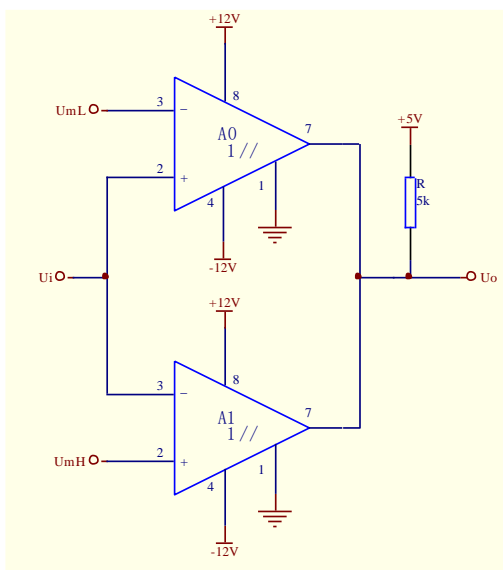

3-2

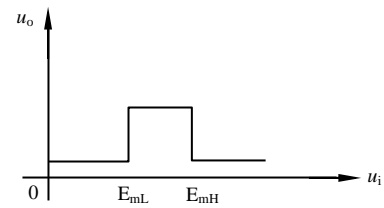


3-3

U_i E_{mL} E_{mH} IC2 IC3

U_i E_{mH} IC2 IC3

E_{mL} U_i E_{mH} IC2 IC3

3-3

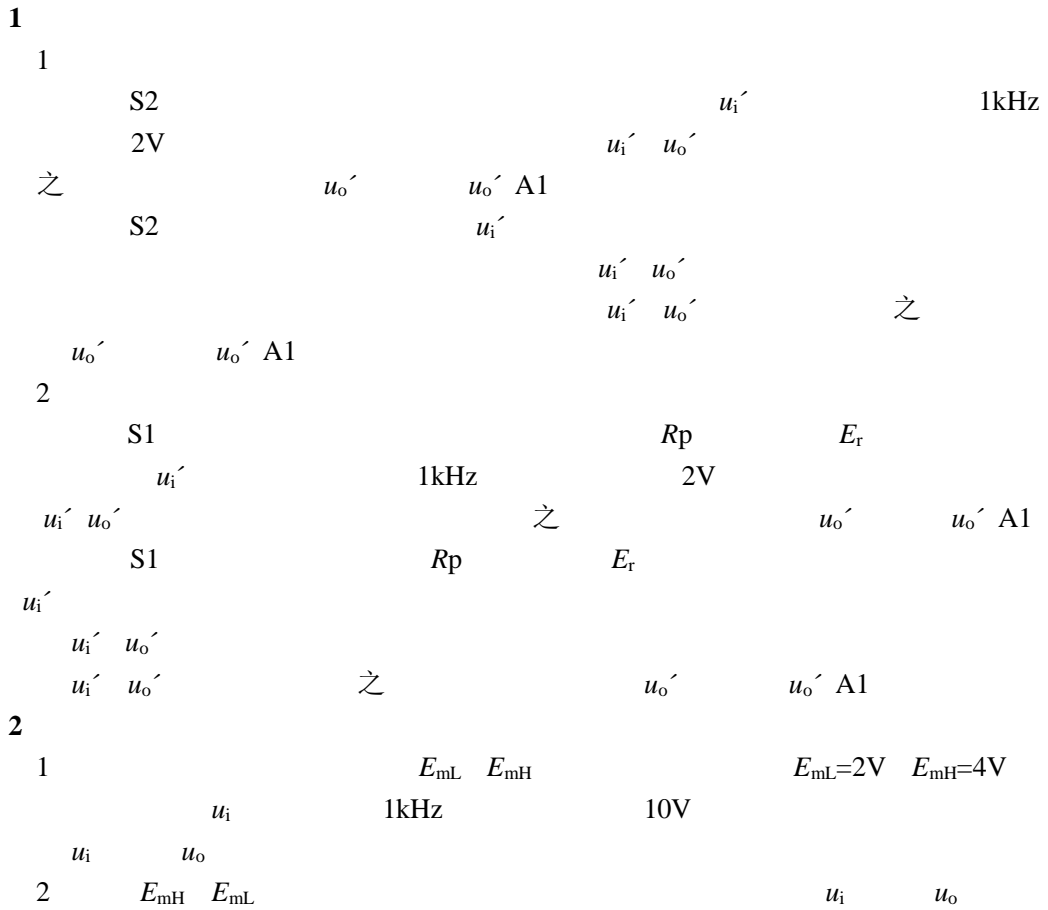

1
2
3

ICL8038

1 ICL8038
 2 ICL8038
 3

1
 2

1 ICL8038

ICL8038

代

IC

ICL8038

IC

之

ICL8038

0.001Hz 500kHz
 0.5

+10V +30V ±5V ±15V
 50ppm/°C

ICL8038

14-DIP

4-1

ICL8038


4-1 ICL8038

1	SINE WAVE SINADJ ₁	6	V ₊	11	V OR AND
2	SINE WAVE OUT	7	FM BIAS	12	SINE WAVE SINADJ ₂
3	TRIANGLE OUT	8	FM SWEEP INPUT	13	NC
4	DUTY CYCLE	9	SQUARE WAVE OUT	14	NC
5	FREQUENCY DFADJ	10	TIMING CAPACITOR		


2 ICL8038

4-1

ICL8038

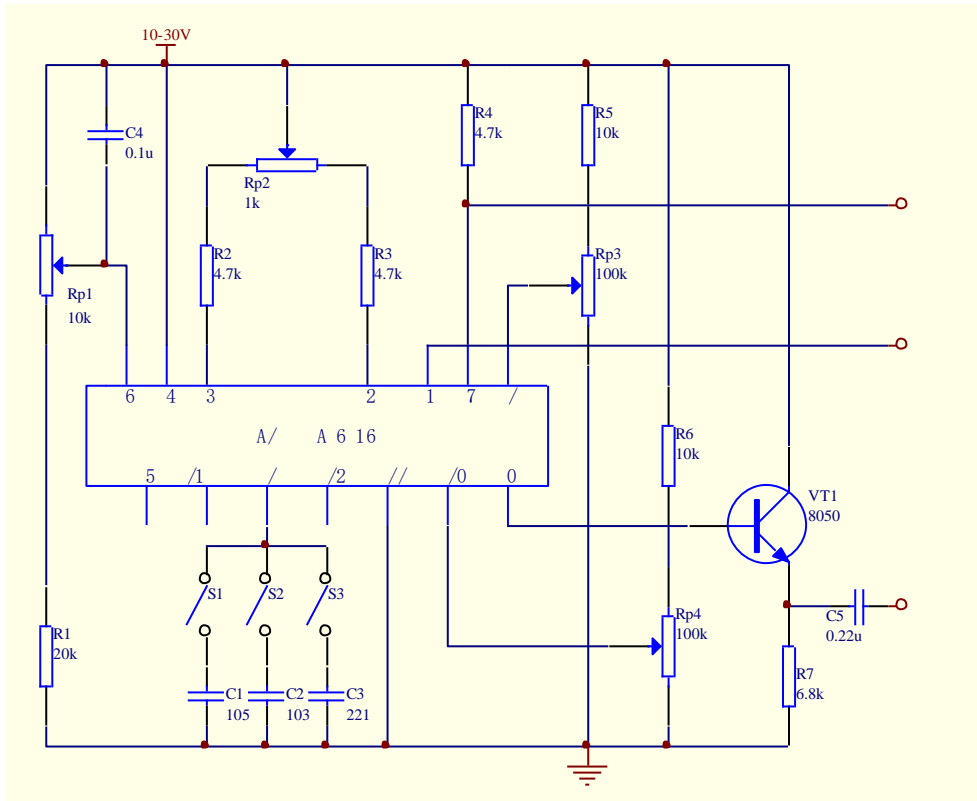

4-1 ICL8038

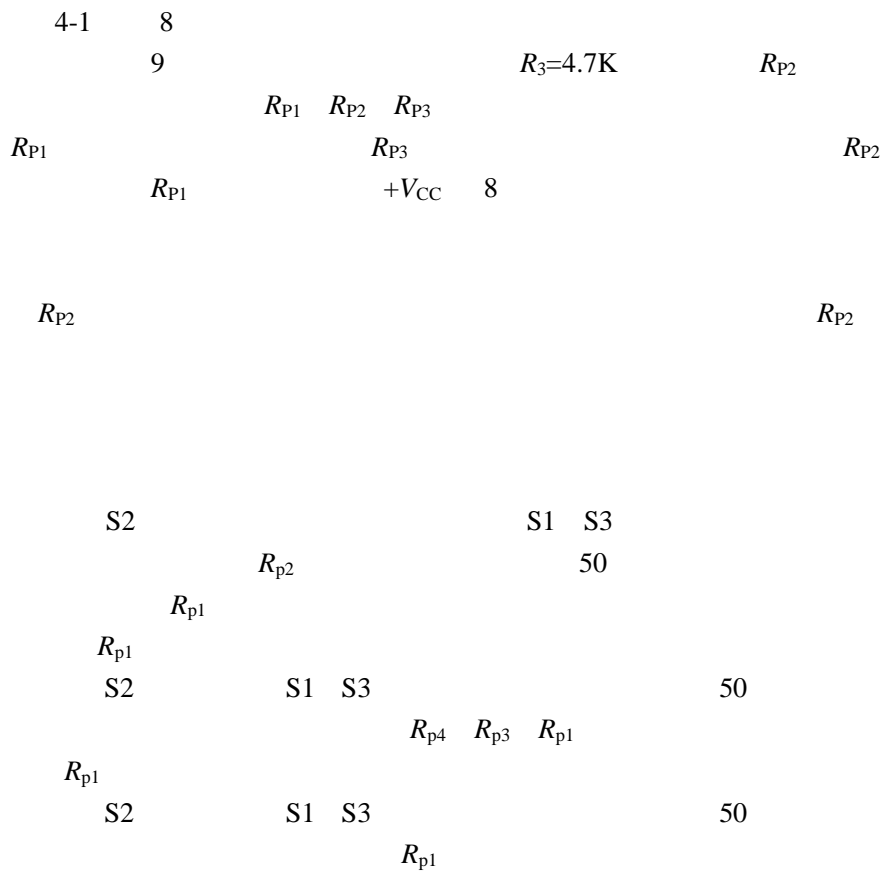

4		3		S1		S2	S3		S2
	S1	S3		S1	S2				R_{p2}
10		90							
5		4		R_{p1}	R_{p2}	R_{p3}	R_{p4}		

1		1	2	3
2		4		
3		5		
4				